


CS 341 – Lab 7

Seven Segment Display

In this lab, you will learn how to use a 7 segment display. We will write to it to display numbers using a decoder chip that simplifies our code. When done, your display should loop through digits 0-9. The starter code can be found [here](#) under Lab 7.

Background Information

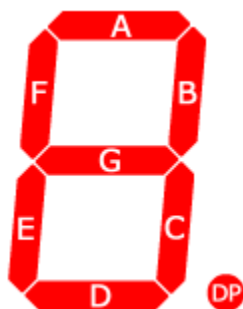Seven Segment Displays are used in many consumer devices like calculators, clocks, watches, counters and microwave ovens. They are made out of LEDs and are low cost devices to display information. They come in a variety of colors and sizes. Some displays have a single digit and others have multiple digits.




Seven segment displays consist of 7 LEDs, called segments, arranged in the shape of an “8” and a dot on the right side of the digit that serves as a decimal point. Each segment is named with a letter A to G, and DP for the decimal point. For example, to display a number 7, the segments A, B and C must be lit up.

To make the matching of digits to segments easier, seven segment display chips come with a 4-bit decoder which maps the digits in binary (e.g. 0 – 9 and some special characters) to the correct segments to display that number. Instead of lighting the groups of segments to form a digit, the user programs the 4-bit decoder to light up the digits as follows:


Decoder Input				Display character
bit 3	bit 2	bit 1	bit 0	
LOW	LOW	LOW	LOW	0
LOW	LOW	LOW	HIGH	1
LOW	LOW	HIGH	LOW	2
LOW	LOW	HIGH	HIGH	3
LOW	HIGH	LOW	LOW	4
LOW	HIGH	LOW	HIGH	5
LOW	HIGH	HIGH	LOW	6
LOW	HIGH	HIGH	HIGH	7
HIGH	LOW	LOW	LOW	8
HIGH	LOW	LOW	HIGH	9
HIGH	LOW	HIGH	LOW	Special Character
HIGH	LOW	HIGH	HIGH	Special Character
HIGH	HIGH	LOW	LOW	Special Character
HIGH	HIGH	LOW	HIGH	Special Character
HIGH	HIGH	HIGH	LOW	Special Character
HIGH	HIGH	HIGH	HIGH	Special Character

In this lab we will make use of 4 digital pins for the decoder: pin 4 for bit 0, pin 5 for bit 1, pin 6 for bit 2, and pin 7 for bit 3.

The Circuit

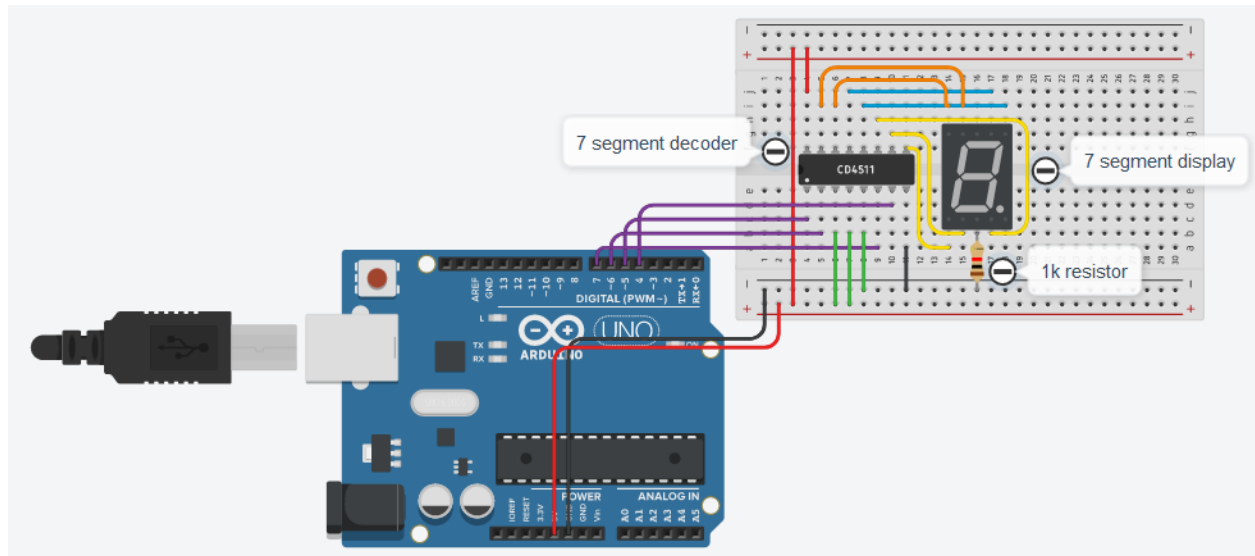

Closeup

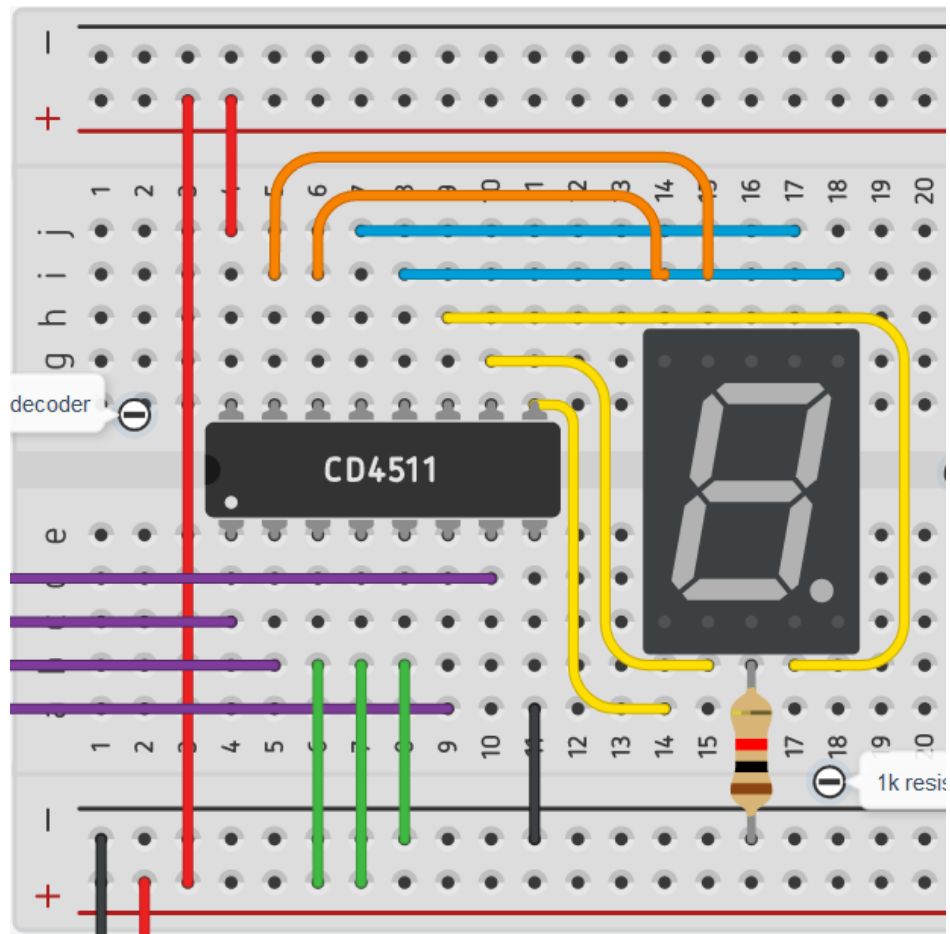

Program the Hardware

Program your 7 segment display so that it counts up from 0. When it gets to 9 it should loop back to 0 again. Make sure your 7 segment display is set to “cathode”. The default is anode which is incorrect.

Lab Report

Please submit your lab through the linux server. For help, see corresponding material [here](#)